

# 1st Lab work: Building an embedded system

Group	1
Student 1	89470 - João Coutinho
Student 2	89472 - João Porto

## Design the interface:

### Calculate the values of resistors associated with the LEDs:

$$\max_i = 40 \text{ mA}, i = 15 \text{ mA}$$

$$v = \text{Power} - \text{VoltageDrop}$$

$$R = \frac{v}{i}$$

#### R\_red:

$$\text{VoltageDrop} = 1.89 \text{ V}$$

$$v = 5 - 1.89 = 3.11 \text{ V}$$

$$R = \frac{3.11}{0.015} = 207.33 \Omega$$

#### R\_green:

$$\text{VoltageDrop} = 2.07 \text{ V}$$

$$v = 5 - 2.07 = 2.93 \text{ V}$$

$$R = \frac{2.93}{0.015} = 195.33 \Omega$$

#### R\_blue:

$$\text{VoltageDrop} = 2.94 \text{ V}$$

$$v = 5 - 2.94 = 2.06 \text{ V}$$

$$R = \frac{2.06}{0.015} = 137.33 \, \Omega$$


**R<sub>yellow</sub>:**

$$VoltageDrop = 2.01 \, V$$

$$v = 5 - 2.01 = 2.99 \, V$$

$$R = \frac{2.99}{0.015} = 199.33 \, \Omega$$

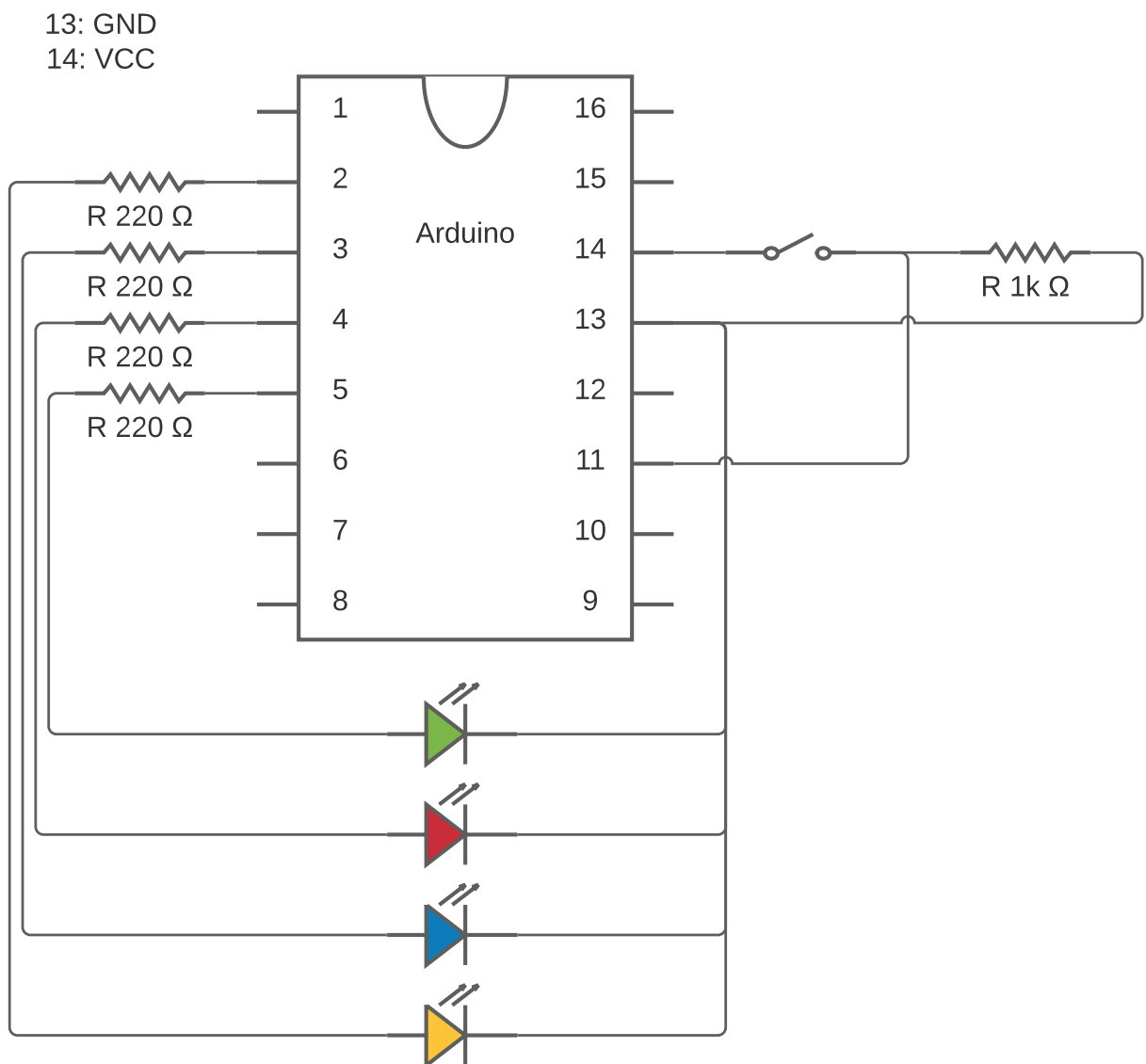**Draw and design the press button interface to the controller:**



**Measure the voltage drops on the LEDs:**

**V<sub>red</sub>:** 1.89 V

**V<sub>green</sub>:** 2.07 V

**V<sub>blue</sub>:** 2.94 V

**V<sub>yellow</sub>:** 2.01 V

**Estimate the power consumption of the interface (the circuit with the resistors and LEDs in the figure) in normal operation:**

$$v = R \times i \Leftrightarrow i = \frac{v}{R}$$

$$p = v \times i = \frac{v^2}{R}$$

**When red LED is lit:**

$$v = 3.11 \text{ V}, R = 220 \Omega$$

$$p = \frac{3.11^2}{220} = 0.04396 \text{ W} = 43.96 \text{ mW}$$

**When green led is lit:**

$$v = 2.93 \text{ v}, R = 220 \Omega$$

$$p = \frac{2.93^2}{220} = 0.03902 \text{ W} = 39.02 \text{ mW}$$

**When blue led is lit:**

$$v = 2.06 \text{ v}, R = 220 \Omega$$

$$p = \frac{2.06^2}{220} = 0.01929 \text{ W} = 19.29 \text{ mW}$$

**When yellow led is lit:**

$$v = 2.99 \text{ v}, R = 220 \Omega$$

$$p = \frac{2.99^2}{220} = 0.04064 \text{ W} = 40.64 \text{ mW}$$

**Max consumption:** 43.96 mW, **Average consumption:**

$$\frac{43.96+39.02+19.29+40.64}{5} = \frac{142.91}{5} = 28.58 \text{ mW}$$

**Program the application:**

## Add your program listing (adequately structured and commented):

```
const int GREEN = 5;
const int RED = 4;
const int BLUE = 3;
const int YELLOW = 2;
const int BUTTON = 11;

void setup()
{
    pinMode(GREEN, OUTPUT);
    pinMode(RED, OUTPUT);
    pinMode(BLUE, OUTPUT);
    pinMode(YELLOW, OUTPUT);
    pinMode(BUTTON, INPUT);
    pinMode(LED_BUILTIN, OUTPUT); // use builtin LED as paused
indicator

    digitalWrite(GREEN, LOW); // turn the LED off (LOW is the
voltage level)
    digitalWrite(RED, LOW); // turn the LED off (LOW is the
voltage level)
    digitalWrite(BLUE, LOW); // turn the LED off (LOW is the
voltage level)
    digitalWrite(YELLOW, LOW); // turn the LED off (LOW is the
voltage level)
}

void loop()
{
    // 1st
    blink(RED, 1000);

    // 2nd
    blink(GREEN, 1000);
```

```

// 3rd
blink(BLUE, 1000);

// 4th
blink(YELLOW, 1000);

// 5th
wait(1000); // wait 1000ms
}

// Function to blink the LED
void blink(int led, long duration)
{
    digitalWrite(led, HIGH); // turn the LED on (HIGH is the voltage
level)
    wait(duration);          // wait 1000ms
    digitalWrite(led, LOW);  // turn the LED off by making the
voltage low
}

// Our interpretation of the guide is that the system remains
paused between button presses
// and not while the button is pressed
void wait(unsigned long duration)
{
    unsigned long current_time = millis();
    bool paused = false;
    delay(10);

    while (millis() - current_time < duration)
    {

        // Toggle paused state when button is pressed
        if (digitalRead(BUTTON) == HIGH)
        {
            paused = !paused;
            duration -= millis() - current_time; // Deduct already
elapsed time from duration

```

```
        delay(250);                                // Buffer wait to allow
button to depress
    }

    // Freeze time when state is paused
    if (paused)
    {
        digitalWrite(LED_BUILTIN, HIGH);
        current_time = millis();
    }
    else
    {
        digitalWrite(LED_BUILTIN, LOW);
    }
}
}
```